

EE2026: DIGITAL DESIGN

Academic Year 2020-2021, Semester 1

LAB 4: Sequential Circuits in Verilog - Part 2

OVERVIEW

This lab is a continuation of Lab 3. In this Lab 4, more applications of sequential circuits will be explored, and this will be the last lab practice before the EE2026 project.

The pre-requisites for this lab are:

- Knowing how to obtain slower clock frequencies from a faster one.
- Brief understanding of the purpose of a D-Flip-Flop (D-FF) in a sequential circuit.

This lab will cover the following:

- Schematic and design of a single pulse circuit, by using two D-FFs with a clock signal.
- Schematic and design of a debounced single pulse circuit, by using two D-FFs with a slow clock signal.
- Incrementing a counter value by 1 when a pushbutton is pressed.
- Multiplying a counter value by 2 when a pushbutton is pressed.

Tasks for this lab include:

- Simulating a single pulse circuit, whereby the D-FFs use a 100 MHz clock.
- Implementing a debounced single pulse circuit, by using a 3 Hz clock, on the Bays 3 development board.
- Observing patterns on the physical LED array, through counters that use the debounced single pulse signal.

GRADED ASSIGNMENT [LUMINUS SUBMISSION: TUESDAY 13th OCTOBER 2020, NOON]:

This is the final lab assignment to test whether you have properly mastered the technical contents from your three previous lab assignments. In this lab 4 assignment, the focus will be more on two very important components for the upcoming project: Integration and Logic

You are strongly encouraged to complete this assignment before the start of Week 8 (Monday 5th October 2020), as the focus will be on the EE2026 project from there on.

Further details are available at the end of this lab manual.

CREATING A SINGLE PULSE OUTPUT [Take 30 minutes before the lab to think how this can be done]

In this section, a single pulse output circuit will be created. The circuit from [Figure 4.1](#), consisting of two D-FFs and an AND gate, can be used to generate a single pulse output signal. The latter will be a synchronised logic true signal that lasts for the duration of one clock cycle.

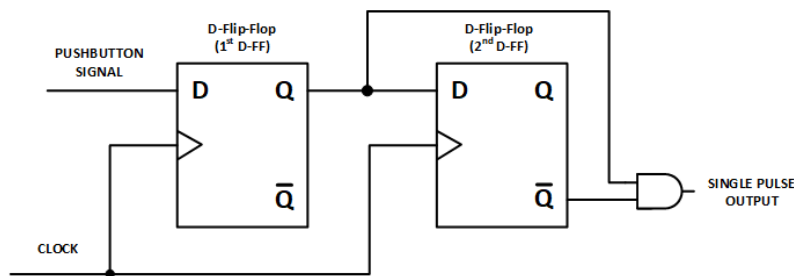


Figure 4.1: Single pulse circuit

The waveform for the single pulse circuit is as shown in *Figure 4.2*

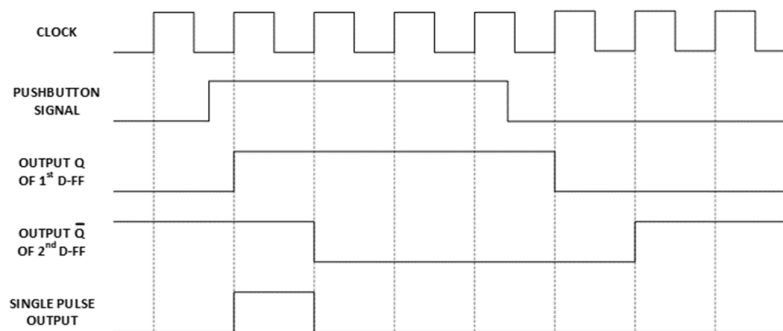


Figure 4.2: Waveform from a single pulse circuit

UNDERSTANDING | TASK 1

Through behavioural modelling in Verilog, the code for a positive-edge triggered D-flip-flop can be created:

Verilog code for a positive-edge triggered D-flip-flop

```

module my_dff(input DFF_CLOCK, D, output reg Q = 0);

    always @ (posedge DFF_CLOCK) begin
        Q <= D;
    end

endmodule

```

Using structural, dataflow and/or behavioural modelling, create the Verilog design for the circuit shown in [Figure 4.1](#). Create the simulation for the single pulse design module, with a simulated 100 MHz clock and appropriate stimuli, to confirm that a single pulse can be obtained. Take note of the time scale in the simulation window, and determine the duration of the single pulse output.

CREATING A DEBOUNCED SINGLE PULSE OUTPUT

On a physical device, the single pulse circuit can also be used to debounce mechanical switch signals. A slower clock, whose time period is longer than the bouncing of the switch signal, is required. Feeding this slower clock signal to the two D-FFs of a single pulse circuit will create a debounced single pulse output, as illustrated in *Figure 4.3*

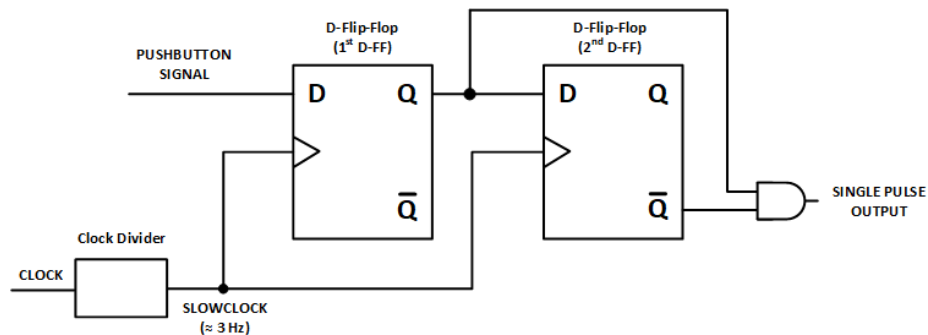


Figure 4.3: Debounced single pulse circuit

The waveform for the debounced single pulse circuit is as shown in *Figure 4.4*

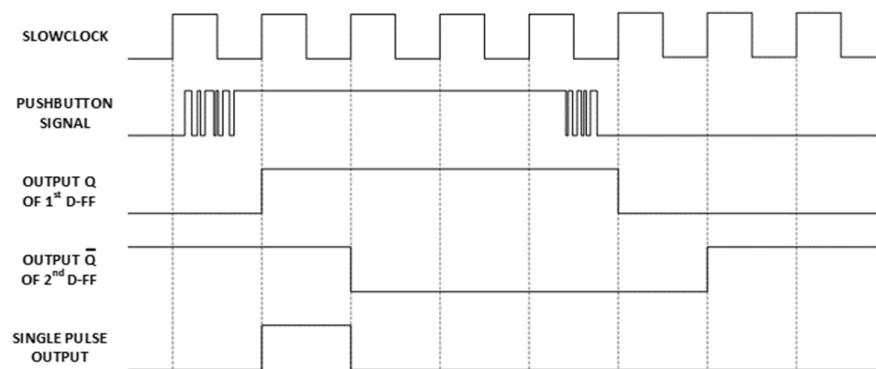


Figure 4.4: Waveform from a debounced single pulse circuit

UNDERSTANDING | TASK 2

Implement the circuit in *Figure 4.3* on the Basys 3 development board, by linking the debounced single pulse output to an LED. Press and hold the pushbutton to see if a single pulse of 1 clock cycle is obtained.

How much of simulated time would be required in order to see the single pulse output in the simulation waveform window?

Can you think of other ways of implementing a debounced single pulse output?

APPLYING THE DEBOUNCED SINGLE PULSE

From **UNDERSTANDING | TASK 2**, it is noted that no matter how long the pushbutton is pressed and held, a single synchronous pulse of only one clock cycle is created. This allows for the creation of a counter whose value can be made to increase by 1 each time a pushbutton is pressed, as such press would result in a positive edge of a single pulse.

UNDERSTANDING | TASK 3

Design an 8-bit counter that makes use of the debounced single pulse output, in order to increase its value by 1 each time the pushbutton is pressed, and for no matter how long the pushbutton is held. Implement the design on the Basys 3 development board, and observe how the physical LED array pattern changes whenever the pushbutton is pressed (and optionally held for a long time). Consider using the code below to detect the rising edge of the single pulse signal:

Partial Verilog code for a count that increments by one at the positive edge of the synchronised single pulse signal

```
// Initialise the initial 8-bit counter value to 8'b0000_0000
always @ (posedge SLOWCLOCK) begin
    if (SINGLE_PULSE_OUTPUT == 1) begin
        my_counter <= my_counter + 1;
    end
end
```

Important: The clock used in the sensitivity list must be exactly the same clock that was used to create the single pulse output

UNDERSTANDING | TASK 4

Shifting the values in a register to the left multiplies the register value by the base value. Create another design for a 16-bit counter, whereby pressing the pushbutton multiplies the value by 2 (Binary / Base-2 system). Implement the design on the Basys 3 development board. You may use the Verilog code template given below:

Partial Verilog code for a count that multiplies by 2 at the positive edge of the synchronised single pulse signal

```
// Initialise the initial 16-bit counter value to 16'h000C;
always @ (posedge SLOWCLOCK) begin
    if (SINGLE_PULSE_OUTPUT == 1) begin
        my_counter <= my_counter << 1;
    end
end
```

Record the values that you see from the LED array in the table below:

	Value from the Physical LED Array	Unsigned Decimal
Original Value	0000 0000 0000 1100	12
1 st Pushbutton Press		
2 nd Pushbutton Press		
3 rd Pushbutton Press		
4 th Pushbutton Press		
5 th Pushbutton Press		
6 th Pushbutton Press		
...		

What kind of pattern do you notice in the values?

What happens for pushbutton presses after the 13th and 14th ones?

UNDERSTANDING | TASK 5

Change your SLOWCLOCK to a 12 Hz clock. What do you notice when the pushbutton is pressed for the counter?

Change your SLOWCLOCK to a 25 MHz clock? What do you notice when the pushbutton is pressed for the counter?

GRADED POST-LAB ASSIGNMENT

Read and understand all the sub-tasks before starting to work on your program.

Complete as much as possible, **in one working bitstream**, within the given deadline. It is much better to have a working program with some completed sub-tasks, instead of submitting a program without a working bitstream.

You may need a few of the operators listed below for the assignment (as well as for the upcoming EE2026 project):

Bitwise Operators		
~	~m	invert each bit of m
&	m & n	AND each bit of m with each bit of n
	m n	OR each bit of m with each bit of n
^	m ^ n	exclusive-OR each bit of m with n
~^ or ^~	m ~^ n	exclusive-NOR each bit of m with n
<<	m << n	shift m left n-times and fill with zeros
>>	m >> n	shift m right n-times and fill with zeros
Unary Reduction Operators		
&	&m	AND all bits in m together (1-bit result)
~&	~&m	NAND all bits in m together (1-bit result)
	m	OR all bits in m together (1-bit result)
~	~ m	NOR all bits in m together (1-bit result)
^	^m	exclusive-OR all bits in m (1-bit result)
~^ or ^~	~^m	exclusive-NOR all bits in m (1-bit result)
Logical Operators		
!	!m	is m not true? (1-bit True/False result)
&&	m && n	are both m and n true? (1-bit True/False result)
	m n	are either m or n true? (1-bit True/False result)
Equality and Relational Operators (return X if an operand has X or Z)		
==	m == n	is m equal to n? (1-bit True/False result)
!=	m != n	is m not equal to n? (1-bit True/False result)
<	m < n	is m less than n? (1-bit True/False result)
>	m > n	is m greater than n? (1-bit True/False result)
<=	m <= n	is m less than or equal to n? (1-bit True/False result)
>=	m >= n	is m greater than or equal to n? (1-bit True/False result)
Identity Operators (compare logic values 0, 1, X, and Z)		
===	m === n	is m identical to n? (1-bit True/False results)
!==	m !== n	is m not identical to n? (1-bit True/False result)
Miscellaneous Operators		
? :	sel?m:n	conditional operator; if sel is true, return m; else return n
{ }	{m, n}	concatenate m to n, creating a larger vector
{ { }	{n { }	replicate inner concatenation n-times
->	-> m	trigger an event on an event data type

Arithmetic Operators		
+	m + n	add n to m
-	m - n	subtract n from m
-	-m	negate m (2's complement)
*	m * n	multiply m by n
/	m / n	divide m by n
%	m % n	modulus of m / n
**	m ** n	m to the power n (new in Verilog-2001)
<<<	m <<< n	shift m left n-times, filling with 0 (new in Verilog-2001)
>>>	m >>> n	shift m right n-times; fill with value of sign bit if expression is signed, otherwise fill with 0 (Verilog-2001)

It is required to complete and fully understand all the five UNDERSTANDING | TASK of lab 4 before starting this assignment. **The accuracy and responsiveness of the pushbuttons will be tested. High accuracy and high responsiveness are required.**

SUB-TASK A [TALLYING]

By default, the program starts with all the active-high switches set to ON (HIGH / 1), LEDs LD0 to LD15 all OFF, and all segments (7 segments + decimal point) of the seven-segment displays OFF. When this tallying sub-system starts, it is required to clearly observe the following sequence of 5 characters on specific seven-segment displays at the specified time steps:

	AN3	AN2	AN1	AN0
Time Step 01	£			
Time Step 02		ⱥ		
Time Step 03			!	
Time Step 04			!	
Time Step 05				Ÿ

Each time step is 0.68 seconds long
(An error of ± 0.1 second is acceptable)

After Time Step 05 has shown the character “Y”, it is required to be able to clearly observe the following, until the user presses the up pushbutton (BTNU):

	AN3	AN2	AN1	AN0
Observation	£	ⱥ	!!	Ÿ

Hint: Repeat Time Step 01 to 05 at a frequency of 762 Hz
(Maximum error of $\pm 5\%$ for frequency is acceptable)

When the user presses the up pushbutton (BTNU) at least once, the following display is to be shown:

AN3	AN2	AN1	AN0
0	0	0	0

Assume that AN0 to AN2 now represent separate rooms. Whenever a person enters the room, one additional horizontal bar is to be lit up, up to a maximum of 3 horizontal bars. The following actions indicate that a person is entering a room:

BTNL (Left pushbutton):	One additional person is entering room AN2
BTNC (Centre pushbutton):	One additional person is entering room AN1
BTNR (Right pushbutton):	One additional person is entering room AN0

At any time during the running of the tallying sub-system, AN3 indicates the total amount of persons in all three rooms, in hexadecimal number format. In this sub-system for tallying, assume that there will not be more than 3 persons per room. An example is shown below, with 2 persons inside room AN2, 3 persons inside room AN1, and 2 persons inside room AN0:

AN3	AN2	AN1	AN0
7	=	≡	=

The user may reset back to 0, the amount of person inside all the rooms by pressing the up pushbutton (BTNU) at any time during the running of the tallying sub-system.

SUB-TASK B [ACTIVE NOTIFICATIONS]

In order to prevent overcrowding and to distribute the amount of people inside the rooms evenly, the following two rules are to be implemented into the tallying sub-system:

- (1) A person can only enter a room if the difference in number of persons inside the room will not be more than 1 (Difference can be 1) after entering the room, when compared to the other rooms
- (2) No two persons can enter the same room one after the other

If any of the above two rules are broken, the person must not be allowed to enter the room.

An active notification in the form of a blinking decimal point and blinking horizontal bar(s) in that specific room the person was trying to enter should occur for a duration of 5.37 seconds (± 0.5 second error is acceptable). The blinking decimal point and blinking horizontal bar(s) occur at a frequency of 6 Hz (Maximum error of $\pm 5\%$ in frequency is acceptable). If the blinking is happening, no person will be allowed to enter any of the rooms until the blinking stops. Example: If the segments in AN2 is blinking, none of three pushbuttons: BTNL, BTN and BTNR, should register any pushbutton presses.

SUB-TASK C [COMPLIANT EVACUATIONS]

In the event of a fire emergency, any persons in any rooms can exit at any time in any order. A fire emergency is triggered when SW0 is set to OFF (LOW / 0). The following actions indicate that a person is evacuating from a room:

BTNL (Left pushbutton):	One person is evacuating room AN2
BTNC (Centre pushbutton):	One person is evacuating room AN1
BTNR (Right pushbutton):	One person is evacuating room AN0

During such fire emergencies, when the total amount of persons in all three rooms combined is zero, the following message should be shown:

AN3	AN2	AN1	AN0
P	A	S	S

SUB-TASK D [DIGITAL INTEGRATED SYSTEM]

A complete system will now be required so that it can be used for the Digital Electronics Lab. Using what you have learnt in the SAFE system from lab 3, a complete Digital Integrated System for Tallying, Active Notifications and Compliant Evacuations is required. The complete SAFE-DISTANCE works as follows:

- (1) As SW0 is ON by default when the program is uploaded, it is required to light up the 16 LEDs in increasing order, that is, from LD0 to LD15. Each additional LED need to wait 0.0836 seconds (± 0.05 second error is acceptable) to light up. None of the LEDs must blink. They must all have fully ON LEDs.
- (2) When all 16 LEDs (LD0 to LD15) are ON, sub-task A occurs
- (3) Sub-task B, if it has been implemented, also runs as part of sub-task A
- (4) Sub-task C is triggered when SW0 is set to OFF. In this complete SAFE-DISTANCE, it is furthermore required for the 16 LEDs to turn OFF in decreasing order (LD15 to LD0). Each additional LED need to wait 0.167 seconds (± 0.05 second error is acceptable) to turn off. If the amount of oxygen runs out in the rooms, that is all the 16 LEDs are OFF, before all persons have left the room, the following message should be shown:

AN3	AN2	AN1	AN0
F	A	I	L

Assume that the program ends there when "PASS" or "FAIL" is shown. If there is a need to re-run the program, set SW0 to ON, and reload the bitstream to run the SAFE-DISTANCE.

LUMINUS SUBMISSION INSTRUCTIONS

- Complete as much required functionalities **as possible within the given deadline**, and ensure that your bitstream has been successfully generated and tested on your Basys 3 development board **BEFORE** archiving your Vivado workspace for LumiNUS upload. No working bitstream is equivalent to no marks (It is best to have some working functionalities / requirements, instead of not having any bitstream at all while trying all requirements)
- It is compulsory to archive your project in a compressed form without any simulation waveforms. In the uploaded archive, the codes (.v files) are important, not the waveforms (.wdb files). **The archive size should not exceed 4 MB in size for lab 4.** Follow the instructions given in the pdf: “Archive Project in Vivado 2018.02”
- **After** following the instructions in “**Archive Project in Vivado 2018.02**”, rename your project archive as indicated in the appendix of this lab manual
- Upload to LumiNUS EE2026 -> Files -> Lab and Project - Materials and Submissions -> Lab 4 Submission
- Download your LumiNUS archive after uploading. **Unzip it / Extract all, and check if you can run your bitstream correctly.** No project files and no working bitstream is equivalent to losing all marks
- The LumiNUS upload must be completed by **Tuesday 13th October 2020, 12:00 P.M. (Noon)**. Do not plan to upload during the grace period of 2 hours
- Late submissions for lab 4 are not accepted. Complete as much required functionalities as possible within the given deadline and in one working program

Plagiarism is penalised with a 100% penalty for all SOURCES and RECIPIENTS

All past and future submissions, and marks, will be reviewed in greater detail, for any person found to have plagiarised

REMEMBER TO NAME YOUR SUBMISSION IN THE REQUIRED FORMAT

ALL THE SUBMISSION INSTRUCTIONS LISTED ABOVE WILL AFFECT YOUR GRADES!

APPENDIX (Renaming submissions just before LumiNUS upload):

It is **compulsory to rename your project archive**, just before LumiNUS upload, as indicated in the table below. Copy your respective “Archive Naming” for the archive, and then replace the “xxxxxxxx” with your student ID number. Do not change any other part of the naming, except the “xxxxxxxx”.

Submission example for project archive: **L4_Fri_AM_Alan Turing_Archive_A0131086Z**

Name	Archive Naming
A AKIL AHAMED	L4 Fri AM A AKIL AHAMED Archive XXXXXXXXX
Abdul Hadi Bin Abdul Samad	L4 Fri AM Abdul Hadi Bin Abdul Archive XXXXXXXXX
Adabelle Lim Ru Leng	L4 Fri AM Adabelle Lim Ru Leng Archive XXXXXXXXX
Alfred Wrong Jia Qing	L4 Fri AM Alfred Wrong Jia Qin Archive XXXXXXXXX
Alvin Goh Jia Hao	L4 Fri AM Alvin Goh Jia Hao Archive XXXXXXXXX
Alvinci Merquita	L4 Wed AM Alvinci Merquita Archive XXXXXXXXX
ANG KENG SIANG	L4 Wed AM ANG KENG SIANG Archive XXXXXXXXX
Aryl Ng Shen Le	L4 Wed AM Aryl Ng Shen Le Archive XXXXXXXXX
Au Yuan Xian	L4 Fri AM Au Yuan Xian Archive XXXXXXXXX
Bai Xiaoru	L4 Fri AM Bai Xiaoru Archive XXXXXXXXX
Bryan Yu Cheng You	L4 Fri AM Bryan Yu Cheng You Archive XXXXXXXXX
Chai Wei Lynthia	L4 Fri AM Chai Wei Lynthia Archive XXXXXXXXX
Cheang Zhi Yi Jordan	L4 Fri AM Cheang Zhi Yi Jordan Archive XXXXXXXXX
Chee Poh Hock	L4 Wed AM Chee Poh Hock Archive XXXXXXXXX
Cheng Wei Qiao	L4 Fri AM Cheng Wei Qiao Archive XXXXXXXXX
Cheung Po Rui Bryan	L4 Fri AM Cheung Po Rui Bryan Archive XXXXXXXXX
CHONG LEE TENG VALENCIA	L4 Wed AM CHONG LEE TENG VALEN Archive XXXXXXXXX
Davian Chan Sze Peng	L4 Fri AM Davian Chan Sze Peng Archive XXXXXXXXX
David Michael Woodside	L4 Fri AM David Michael Woodsi Archive XXXXXXXXX
ELJER CHUA	L4 Fri AM ELJER CHUA Archive XXXXXXXXX
FANG XINJIA	L4 Fri AM FANG XINJIA Archive XXXXXXXXX
Fidel Tan Yan Sheng	L4 Fri AM Fidel Tan Yan Sheng Archive XXXXXXXXX
Foo Fang Kiang	L4 Fri AM Foo Fang Kiang Archive XXXXXXXXX
Gao Zhixuan	L4 Fri AM Gao Zhixuan Archive XXXXXXXXX
Giam Xiong Yao	L4 Fri AM Giam Xiong Yao Archive XXXXXXXXX
Gillian Ho Xin Ying	L4 Fri AM Gillian Ho Xin Ying Archive XXXXXXXXX
Goh Jia Hong Edwin	L4 Wed AM Goh Jia Hong Edwin Archive XXXXXXXXX
Guinne Teresa Sng Yu Lin	L4 Fri AM Guinne Teresa Sng Yu Archive XXXXXXXXX
Hariharan Hadrian S/O Subramaniam	L4 Fri AM Hariharan Hadrian S Archive XXXXXXXXX
HO MING JUN	L4 Wed AM HO MING JUN Archive XXXXXXXXX
Ho Yi Shu Keon	L4 Wed AM Ho Yi Shu Keon Archive XXXXXXXXX
Hou Yinjiayi	L4 Fri AM Hou Yinjiayi Archive XXXXXXXXX
Ian Isaiah Tan Jun Wei	L4 Fri AM Ian Isaiah Tan Jun W Archive XXXXXXXXX
Jacob Zhang Zhiqiang	L4 Wed AM Jacob Zhang Zhiqiang Archive XXXXXXXXX
JEROME TEO SZE YONG	L4 Wed AM JEROME TEO SZE YONG Archive XXXXXXXXX
Jonathan Ang Xu Wen	L4 Wed AM Jonathan Ang Xu Wen Archive XXXXXXXXX
JONATHAN KHOO TENG YANG	L4 Fri AM JONATHAN KHOO TENG Y Archive XXXXXXXXX
Kabeta Takuma	L4 Wed AM Kabeta Takuma Archive XXXXXXXXX
Khoo Wu Jian Samuel	L4 Wed AM Khoo Wu Jian Samuel Archive XXXXXXXXX
KIM JOOHWAN	L4 Fri AM KIM JOOHWAN Archive XXXXXXXXX
Lau Wai Kit	L4 Wed AM Lau Wai Kit Archive XXXXXXXXX
LEE KE HUI	L4 Wed AM LEE KE HUI Archive XXXXXXXXX
Lee Shao Yu	L4 Wed AM Lee Shao Yu Archive XXXXXXXXX
Lek Ju Ying	L4 Wed AM Lek Ju Ying Archive XXXXXXXXX
Leong Ka Weng, Rachelle	L4 Fri AM Leong Ka Weng Rache Archive XXXXXXXXX
LEW POH CHEN, DOUGLAS	L4 Fri AM LEW POH CHEN DOUGLA Archive XXXXXXXXX
Long Deng Jie	L4 Wed AM Long Deng Jie Archive XXXXXXXXX
Markus Lim Yi Qin	L4 Wed AM Markus Lim Yi Qin Archive XXXXXXXXX
Mohamad Adam Bin Mohamad Yazid	L4 Wed AM Mohamad Adam Bin Moh Archive XXXXXXXXX
Muhammad Irfan Bin Zakaria	L4 Wed AM Muhammad Irfan Bin Z Archive XXXXXXXXX
Myat Thwe Naing	L4 Wed AM Myat Thwe Naing Archive XXXXXXXXX
Ng Etek	L4 Wed AM Ng Etek Archive XXXXXXXXX
Noorhakim Bin Jasman	L4 Wed AM Noorhakim Bin Jasman Archive XXXXXXXXX
NUR SYADIAH BTE LUTFI	L4 Fri AM NUR SYADIAH BTE LUT Archive XXXXXXXXX
ONG WEI SHENG	L4 Fri AM ONG WEI SHENG Archive XXXXXXXXX
PANG JUN WEN, ADRIC	L4 Fri AM PANG JUN WEN ADRIC Archive XXXXXXXXX
PUN ZE YONG	L4 Wed AM PUN ZE YONG Archive XXXXXXXXX
Qiang Zhuang	L4 Wed AM Qiang Zhuang Archive XXXXXXXXX
QIU YI WEN	L4 Fri AM QIU YI WEN Archive XXXXXXXXX
R M RAAJAMANI	L4 Fri AM R M RAAJAMANI Archive XXXXXXXXX
RIZAVUR RAHMAN FASLUR RAHMAN	L4 Fri AM RIZAVUR RAHMAN FASLU Archive XXXXXXXXX
Ryan Tan Jun Hao	L4 Wed AM Ryan Tan Jun Hao Archive XXXXXXXXX
Saw Wee Kiat	L4 Wed AM Saw Wee Kiat Archive XXXXXXXXX
SIM BOWEN	L4 Fri AM SIM BOWEN Archive XXXXXXXXX
TAM LI NA	L4 Fri AM TAM LI NA Archive XXXXXXXXX
Tan Javen	L4 Wed AM Tan Javen Archive XXXXXXXXX
Tan Kai Hao Andrew	L4 Wed AM Tan Kai Hao Andrew Archive XXXXXXXXX
Tan Suet Ying	L4 Fri AM Tan Suet Ying Archive XXXXXXXXX
Tan Yeung Ming Sean Eugene	L4 Wed AM Tan Yeung Ming Sean Archive XXXXXXXXX
Teoh Yi Zheng	L4 Fri AM Teoh Yi Zheng Archive XXXXXXXXX
Tey Zi Le	L4 Wed AM Tey Zi Le Archive XXXXXXXXX
Thet Ke Min, Sonia	L4 Wed AM Thet Ke Min Sonia Archive XXXXXXXXX
Trina Wern Qin Rong	L4 Fri AM Trina Wern Qin Rong Archive XXXXXXXXX
Venessa Chee Li Lin	L4 Fri AM Venessa Chee Li Lin Archive XXXXXXXXX
WANG HUA CHEN	L4 Fri AM WANG HUA CHEN Archive XXXXXXXXX
Wee Cheng Yuan Andrew	L4 Wed AM Wee Cheng Yuan Andre Archive XXXXXXXXX
Wee Xin Ze	L4 Wed AM Wee Xin Ze Archive XXXXXXXXX
Yeo Zhong Kang Dennis	L4 Wed AM Yeo Zhong Kang Denni Archive XXXXXXXXX
ZHONG SHUHAO	L4 Fri AM ZHONG SHUHAO Archive XXXXXXXXX