

EE2026: DIGITAL DESIGN

Academic Year 2020-2021, Semester 1

LAB 3: Sequential Circuits in Verilog - Part 1

OVERVIEW

A sequential circuit is one where the outputs depend on the current inputs and the sequence of past inputs. As a result, a sequential circuit has memory, also called states. In this lab, some basic sequential circuits will be designed to make an LED blink at various speeds.

The pre-requisites for this lab are:

- A very good understanding and application of dataflow modelling and structural modelling in designing modules.
- Knowing how to use the Vivado IDE well.
- Familiarity and knowledge on how to use “*Set as Top*”, “*reg*” and “*wire*”.

This lab will cover the following:

- Introduction to the implementation of a 1-bit two-to-one multiplexer.
- Using a signal that inverts itself periodically, which shall be called **CLOCK**.
- Making a physical LED blink by using the Basys 3 development board clock signal.

Tasks for this lab include:

- Understanding a 1-bit two-to-one multiplexer that can be used in the graded post-lab assignment.
- Creating a slower clock from a faster clock.
- Having a physical LED blink noticeably on the Basys 3 development board, by using the slower clock.
- Using a switch to make a physical LED blink at two different speeds on the Basys 3 development board.

GRADED ASSIGNMENT [LUMINUS SUBMISSION: WEDNESDAY 23rd SEPTEMBER 2020, NOON]:

- Display periodically changing characters on the 7-segment displays of the Basys 3 development board

Further details are available at the end of this lab manual.

1-BIT TWO-TO-ONE MULTIPLEXER [To attempt before the lab session – Not covered in lab]

A multiplexer (MUX) is a combinational circuit that connects one of its input signals to the output, based on the control signal. A simple 1-bit two-to-one mux, with inputs **A**, **B**, control signal **S**, and output **Z**, is illustrated as a functional block diagram, together with its simplified truth table, in **Figure 3.1**.

 


Figure 3.1: Functional block diagram and truth table of a 1-bit two-to-one multiplexer

UNDERSTANDING | TASK 1

A quick way to implement the Verilog code for a 1-bit two-to-one multiplexer is using the conditional syntax:


condition ? expression1 : expression2;

Notice in the schematic, how the code is automatically recognised as a MUX.


Verilog code for 1-bit two-to-one mux, using the dataflow method

```
module my_2_to_1_mux (input A, B, S, output Z);  
    assign Z = S ? B : A; // assign B to Z if S = 1 or assign A to Z if S = 0;  
endmodule
```

 RTL schematic for the 1-bit two-to-one mux



 Synthesised design schematic for the 1-bit two-to-one mux




Fill in the truth table for the **LUT3**, as extracted from the synthesised design schematic for the 1-bit two-to-one mux:

Explain how the truth table for the **LUT3** matches that of the truth table indicated in **Figure 3.1**:

THE BLINKING LED [To attempt before the lab session]

A simple blinking LED is required to be implemented on the FPGA. To do this, a new signal, **CLOCK**, will be introduced.

The **CLOCK** signal is an external input signal that resembles a square wave of 50% duty cycle. If this **CLOCK** signal is connected directly to a physical LED, the latter will light up when the signal is HIGH, and will switch off when the signal is LOW, as illustrated in **Figure 3.2**.

 

*Figure 3.2: A **CLOCK** signal with 50% duty cycle*

A simple dataflow description in Verilog for a blinky module is written first, followed by a simulation source to verify the design. To create the square wave, or **CLOCK** signal, in the simulation source, a new section of codes will now be introduced:


Verilog code for blinky, using the dataflow method

```
module blinky (input CLOCK, output LED);  
    assign LED = CLOCK;  
endmodule
```

Simulation source code to test the blinky design

```
`timescale 1ns / 1ps  
module test_blinky( );  
    reg CLOCK; wire LED;  
  
    blinky dut (CLOCK, LED);  
  
    initial begin  
        CLOCK = 0;  
    end  
  
    always begin  
        #5 CLOCK = ~CLOCK;  
    end  
  
endmodule
```

 Expected simulation waveform for the blinky design



UNDERSTANDING | TASK 2

Based on the Verilog code and simulation results, check your understanding by answering the following questions:

1. What is the unit of time being used in the simulation source?

2. Every 5 units of time, the value of **CLOCK** is being inverted. What is the clock frequency being used in this simulation?

3. What would happen if the testbench code **CLOCK = 0** is removed?

For the hardware implementation, instead of using an external signal generator for the **CLOCK** signal to the Artix-7 FPGA, the Basys 3 development board includes a single 100 MHz clock generator connected to pin W5 of the Artix-7 FPGA.

Using the original contents of the **Basys3_Master.xdc** in your constraint file, follow these steps:

1. Uncomment lines 7 to 9 to create a clock signal of 100 MHz with 50% duty cycle. If required, rename the signal to the name used in your **blinky** code. In our example, the name **CLOCK** was used, and the final changes may look similar to **Figure 3.3**.
2. Configure the output signal **LED** that is present in your **blinky** code (or the name chosen by you while writing the code) by linking it to any physical LED on the Basys3 development board.

```
1 ## This file is a general .xdc for the Basys3 rev B board
2 ## To use it in a project:
3 ## - uncomment the lines corresponding to used pins
4 ## - rename the used ports (in each line, after get_ports) according to the top level signal names in the project
5
6 ## Clock signal
7 set_property PACKAGE_PIN W5 [get_ports CLOCK]
8 set_property IOSTANDARD LVCMOS33 [get_ports CLOCK]
9 create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports CLOCK]
10
11 ## Switches
12 set_property PACKAGE_PIN V17 [get_ports {sv[0]}]
13 set_property IOSTANDARD LVCMOS33 [get_ports {sv[0]}]
14 set_property PACKAGE_PIN V16 [get_ports {sv[1]}]
15 set_property IOSTANDARD LVCMOS33 [get_ports {sv[1]}]
```

Figure 3.1: Modifying your constraint file, based on the contents of the **Basys3_Master.xdc**

UNDERSTANDING | TASK 3

You may optionally generate the bitstream and upload your code to the Basys3 development board. What do you “notice” about the “blinking” LED?

THE NOTICEABLE BLINKING LED

To be able to observe a blinking LED at a frequency that is visible to the human eyes, modifications need to be done to the Verilog code. Let us introduce a temporary variable **COUNT** that is incremented by 1 at every rising edge (transition from low to high, and also called a positive edge) of the **CLOCK** signal, as shown in **Figure 3.4**. By making use of **COUNT**, a lower frequency signal can be obtained, while the Verilog code for **COUNT** can be created by using the behavioural method of modelling.

 


Figure 3.4: Increasing **COUNT** at each rising edge of **CLOCK**

Verilog code for a slower blinky, using behavioural modelling

```
module slow_blinky_module (input CLOCK);  
    reg [3:0] COUNT = 4'b0000;  
  
    always @ (posedge CLOCK) begin  
        COUNT <= COUNT + 1;  
    end  
  
endmodule
```


UNDERSTANDING | TASK 4

Create a simulation source for the **slow_blinky_module** design, and observe the waveform of signal **COUNT**.

[NOTE] Analysing a variable in the simulation waveform window


By default, the simulation window only shows the waveforms of input and output signals. To see the waveforms of variables during the simulation, such as the variable **COUNT**:

 1. Select the **dut** under the simulation module being used
2. In the **Objects** window, right click on the **COUNT** variable
3. Choose **Add To Wave Window**




After adding the variable **COUNT** to the wave window, the current simulation needs to be re-run. Follow these steps:

 1. Restart the simulation
2. Set the simulation time and units
3. Run the simulation for the amount of time set in step 2



 The **COUNT** variable can then be expanded by clicking on the + symbol to the left of **COUNT**. This allows for every individual bit to be observed as independent waveforms:



State the frequency of **COUNT[3]**, **COUNT[2]**, **COUNT[1]** and **COUNT[0]**: _____, _____, _____, _____

UNDERSTANDING | TASK 5 * Warning: Do not simulate the code. Why? *

Using the knowledge and coding obtained from **UNDERSTANDING | TASK 3** and **UNDERSTANDING | TASK 4**, calculate the minimum size of **COUNT** and the bit number which will allow a clock output of around 0.75 Hz.

Minimum of bits required for **COUNT**: _____ Bit number of **COUNT**: _____

Name that waveform with the frequency of 0.75 Hz as **SLOWCLOCK_A**. Modify the **slow_blinky_module** design, and implement the LED blinking at a frequency of around 0.75 Hz on the Basys 3 development board.

UNDERSTANDING | TASK 6

In the **slow_blinky_module**, insert the following line of code in the always block:


```
always @ (posedge CLOCK) begin
    COUNT <= COUNT + 1;
    LED <= ( COUNT == 4'b0000 ) ? ~LED : LED ;
end
```

Do additional modifications in the **slow_blinky_module** and the testbench code, and simulate the **slow_blinky_module** design.

[NOTE] Hints on the modifications related to **slow_blinky_module**

- ▶ **LED** is an output signal of the design module
- ▶ A signal declared as **reg** can be reused within the design module. An example is an output signal that needs to be reused as input within the design module
- ▶ A design module signal declared as **reg** can be given an initial value, especially if toggling is involved

 If the codes have been correctly written, a simulation waveform similar to what is shown below can be obtained:



Observe the waveform that you have obtained in your simulation window, and calculate the frequency of the signal **LED**:

$f =$ _____ MHz

From your understanding of the multiplexer, state what the following line of code means:

```
LED <= ( COUNT == 4'b0000 ) ? ~LED : LED ;
```

UNDERSTANDING | TASK 7 * *Warning: Do not simulate the code. Why?* *

Using the knowledge and coding obtained from **UNDERSTANDING | TASK 6**, calculate the number of bits for **COUNT** which will allow **LED** to have a frequency of around 0.75 Hz.

Number of bits required for **COUNT**: _____

Name that waveform with the frequency of 0.75 Hz as **SLOWCLOCK_B**. Modify the **slow_blinky_module** design, and implement the LED blinking at a frequency of around 0.75 Hz on the Basys 3 development board.

Finally, modify and implement the Verilog code such that there are two blinking speeds for the LED based on the state of a switch:

- If the switch is in the OFF position, the LED should blink at a frequency of around 0.75 Hz
- If the switch is in the ON position, the LED should blink at a frequency of around 1.50 Hz

One way to accomplish this task is to use multiplexers in Verilog, as learnt earlier in this lab manual. It may also be implemented using other methods that involve conditional statements.

GRADED POST-LAB ASSIGNMENT

SUB-TASK A [STARTING SEQUENCE]

For this post-lab graded assignment, a simplified system to fill or empty a storage container is required. In your program, all characters appearing on the seven-segment displays must follow *Table A*, as shown below:

Character	Aa	Bb	Cc	Dd	Ee	Ff	Gg	Hh	Ii	Jj	Kk	Ll	Mm
Seven-segment display	A	b	C	d	E	F	G	H	I	J	K	L	M
Character	Nn	Oo	Pp	Qq	Rr	Ss	Tt	Uu	Vv	Ww	Xx	Yy	Zz
Seven-segment display	n	O	P	q	r	S	t	U	V	W	X	Y	Z
Character	0	1	2	3	4	5	6	7	8	9	-	.	@
Seven-segment display	0	1	2	3	4	5	6	7	8	9	-	.	@

Table A

Throughout your program, the following seven-segment displays must be activated depending on the **1st (First)** rightmost numerical value of your student matriculation number, as indicated in *Table B*:

Seven-segment displays that are required to be always ON or OFF				
1 st (First) rightmost numerical value of your student matriculation number	AN3 Display	AN2 Display	AN1 Display	AN0 Display
0	ON	ON	ON	ON
1	ON	ON	ON	OFF
2	ON	ON	OFF	ON
3	ON	ON	OFF	OFF
4	ON	OFF	ON	ON
5	ON	OFF	ON	OFF
6	ON	OFF	OFF	ON
7	ON	OFF	OFF	OFF
8	OFF	ON	ON	ON
9	OFF	ON	ON	OFF

Table B

At the start of your program, all switches must be in the OFF position, and all LEDs are OFF. When your program starts, there is a sequence of character that needs to be seen. Depending on your **3rd (Third)** rightmost numerical value of your student matriculation number, it is required that the character shown on the activated seven-segment displays follows the sequence indicated in *Table C* below, with each update in character occurring at the indicated frequency.

3 rd (Third) rightmost numerical value of your student matriculation number	Sequence of characters that need to be seen and repeated non-stop, until SW15 is set to ON	Frequency of character update (See Note 1 and Note 2)
0	0 ▶ 1 ▶ 2 ▶ 3 ▶ 4 ▶ 5 ▶ 6 ▶ Repeat again from 0	6.00 Hz
1	1 ▶ 2 ▶ 3 ▶ 4 ▶ 5 ▶ Repeat again from 1	1.50 Hz
2	2 ▶ 3 ▶ 4 ▶ 5 ▶ 6 ▶ 7 ▶ 8 ▶ Repeat again from 2	6.00 Hz
3	3 ▶ 4 ▶ 5 ▶ 6 ▶ 7 ▶ 8 ▶ Repeat again from 3	6.00 Hz
4	4 ▶ 5 ▶ 6 ▶ 7 ▶ Repeat again from 4	1.50 Hz
5	5 ▶ 4 ▶ 3 ▶ 2 ▶ 1 ▶ 0 ▶ Repeat again from 5	6.00 Hz
6	6 ▶ 5 ▶ 4 ▶ 3 ▶ 2 ▶ 1 ▶ 0 ▶ Repeat again from 6	6.00 Hz
7	7 ▶ 6 ▶ 5 ▶ 4 ▶ 3 ▶ 2 ▶ Repeat again from 7	1.50 Hz
8	8 ▶ 7 ▶ 6 ▶ 5 ▶ Repeat again from 8	1.50 Hz
9	9 ▶ 8 ▶ 7 ▶ 6 ▶ 5 ▶ 4 ▶ 3 ▶ 2 ▶ Repeat again from 9	6.00 Hz

Table C

Note 1: An error ± 0.25 Hz for the frequency is acceptable

Note 2: Use a stopwatch to test if you are using the correct frequency

SUB-TASK B [SWITCH ACTIVATED FILLING AND EMPTYING]

When SW15 is set to ON, the system changes to a SAFE mode. Assume that the user will not turn OFF SW15 after it has been turned ON. In other words, SW15 will remain ON throughout the remaining parts of the program.

In SAFE mode, the seven segment displays stop showing the starting sequence of characters from sub-task A, and instead show a certain character based on the current amount of LEDs (From LD0 to LD15) being on, as indicated in *Table D* below:

Number of LEDs that are currently ON	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
Character to show on the activated seven segment displays	E	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F	F.

Table D

Anytime during SAFE mode, the user can make SW0 ON or OFF

When SW0 is ON, the amount of LEDs that are turned ON is increased by one for each clock cycle of frequency f_{ON} , in the direction from LD0 to LD15. The 16th LED (LD15) that is ON is required to blink at a frequency f_{BLINK} . When LD0 to LD14 are ON, and LD15 is blinking, nothing else happens to the 16 LEDs unless the user changes the state of SW0 to OFF. It is not required to make the seven-segment displays blink when 16 LEDs are ON (only LED LD15 must blink).

When SW0 is OFF, the amount of LEDs that are ON is decreased by one for each clock cycle of frequency f_{OFF} , in the direction from LD15 to LD0. When all 16 LEDs are OFF, nothing happens to the 16 LEDs, unless the user changes the state of SW0 to ON.

The frequencies used during SAFE mode are dependent on the 1st (First) rightmost numerical value of your student matriculation number, as tabulated in *Table E* below:

1 st (First) rightmost numerical value of your student matriculation number	Frequency, f_{ON} (See Note 3 and Note 4)	Frequency, f_{OFF} (See Note 3 and Note 4)	Frequency, f_{BLINK} (See Note 3 and Note 4)
0	0.75 Hz	3.00 Hz	6.00 Hz
1	3.00 Hz	0.75 Hz	6.00 Hz
2	0.75 Hz	3.00 Hz	6.00 Hz
3	3.00 Hz	0.75 Hz	6.00 Hz
4	0.75 Hz	3.00 Hz	6.00 Hz
5	6.00 Hz	0.75 Hz	3.00 Hz
6	1.50 Hz	6.00 Hz	3.00 Hz
7	6.00 Hz	0.75 Hz	3.00 Hz
8	1.50 Hz	6.00 Hz	3.00 Hz
9	6.00 Hz	0.75 Hz	3.00 Hz

Table E

Note 1: An error ± 0.25 Hz for the frequency is acceptable

Note 2: Use a stopwatch to test if you are using the correct frequency

Furthermore, anytime during SAFE mode, when the user makes SW1 to be ON, no additional LEDs can turn ON or OFF, regardless of whether SW0 is ON or OFF. If SW1 is turned OFF, SAFE mode behaves as per normal.

EXAMPLE BASED ON YOUR STUDENT MATRICULATION CARD NUMBER

If a student has matriculation number "A0002809N" then:

- 1st right-most digit is 9:

Only the middle 2 seven-segment displays out of the 4 seven-segment displays will be ON throughout the running of the program

Frequency, $f_{ON} = 6.00$ Hz (One LEDs turn ON every 0.167 second)


Frequency, $f_{OFF} = 0.75$ Hz (One LEDs turn OFF every 1.333 seconds)

Frequency, $f_{BLINK} = 3.00$ Hz (LD15 will turn ON or OFF every 0.333 second)

- 3rd right-most digit is 8:

Starting sequence is 8 ▶ 7 ▶ 6 ▶ 5 ▶ 8 ▶ 7 ▶ 6 ▶ 5 ▶ 8 ▶ 7 ▶ 6 ▶ 5 ▶ 8 ▶ 7 ▶ 6 ▶ 5 ▶ 8 ...

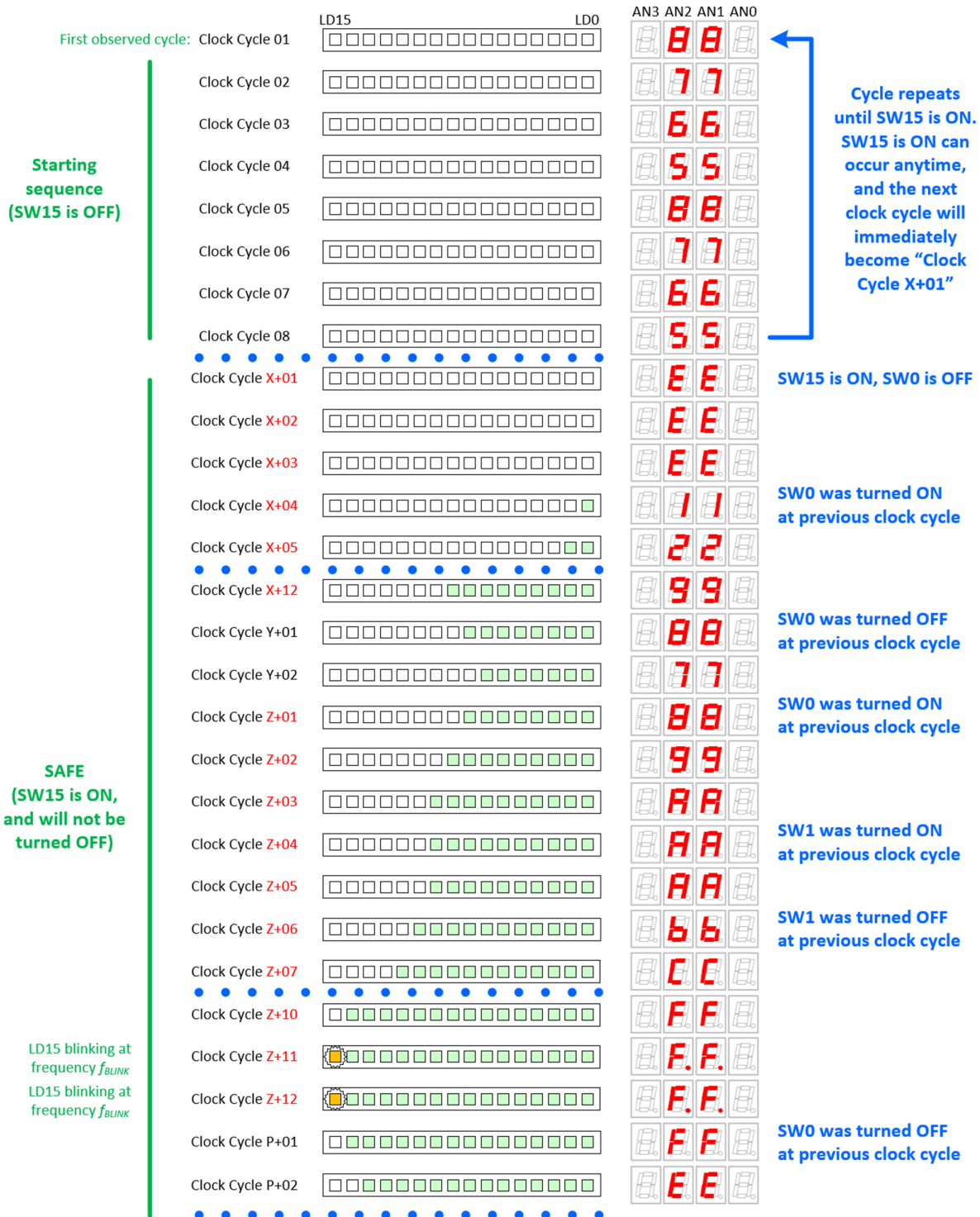Character changes at a frequency of 1.50 Hz (Character changes every 0.667 seconds)



HINTS

- Complete and understand **UNDERSTANDING | TASK 7** clearly before working on this assignment
- Excellent mastery of structural modelling and instantiation is recommended, to properly send signals from one instance to other instances
- Creating different modules for different functions, and then simulating them before instantiating them in a main module will make complex systems easier to debug
- Use multiplexers to select between different clock signals coming from multiple clock dividers
- In Lab 1, single-bit was used for each signal, and information regarding the seven-segment displays were given as well. In Lab 2, multi-bits signals were taught. From this stage onwards, use one set of multi-bits signal to connect to the seven-segments and decimal point, and another set of multi-bit signals to connect to the four seven-segment displays
- A counter whose value can change at each clock cycle can be considered. For example, that counter can count 0, 1, 2, 3, 0, 1, 2, 3 etc ... Following that, if-else statements, multiplexers, or case statement that indicates what to do at each specific counter value can be created

Case statements are recommended here, and the case statement template is given below.

```
case (expression)
  case_item: statement or statement_group
  case_item: statement or statement_group
  default: statement or statement_group
endcase
```

- An example in using case is given below. Note that case statements (if-else statements also) must lie within an always block:

```
always @ (posedge clk_25_mhz)
begin
  case (counter_value)
    2'd0:
      begin
        my_value_a <= 20;
        my_value_b <= 40;
      end
    2'd1:
      begin
        my_value_a <= 100;
        my_value_b <= 200;
      end
    2'd2: my_value_c <= 5;
    default: my_value_d <= 9;
  endcase
end
```

- **Be careful of parallel execution of the always blocks. Multi-driven nets indicate that there are conflicting values being given to the same signal from different always blocks.** For example, one cannot tell a signal to increase at a time instant t, and at that same time instant t, telling it to decrease
- Refer to <http://tiny.cc/ee2026wiki> for more details on commonly encountered errors.

LUMINUS SUBMISSION INSTRUCTIONS

- Complete as much required functionalities **as possible within the given deadline**, and ensure that your bitstream has been successfully generated and tested on your Basys 3 development board **BEFORE** archiving your Vivado workspace for LumiNUS upload. No working bitstream is equivalent to no marks (It is best to have some working functionalities / requirements, instead of not having any bitstream at all while trying all requirements)
- It is compulsory to archive your project in a compressed form without any simulation waveforms. In the uploaded archive, the codes (.v files) are important, not the waveforms (.wdb files). **The archive size should not exceed 2 MB in size for lab 3.** Follow the instructions given in the pdf: "Archive Project in Vivado 2018.02"
- **After** following the instructions in "Archive Project in Vivado 2018.02", rename your project archive as indicated in the appendix of this lab manual.
- Upload to LumiNUS EE2026 -> Files -> Lab and Project - Materials and Submissions -> Lab 3 Submission
- Download your LumiNUS archive after uploading. **Unzip it / Extract all, and check if you can run your bitstream correctly.** No project files and no working bitstream is equivalent to losing all marks
- The LumiNUS upload must be completed by **Wednesday 23rd September 2020, 12:00 P.M. (Noon)**. Do not plan to upload during the grace period of 2 hours
- A penalty of 25% applies for late submissions of up to 1 week.
- The late submission folder closes 1 week after the original deadline. Late submissions are not accepted if you have already submitted on time, or if grading has already started on an earlier submitted file. The late submission folder will be located at: LumiNUS EE2026 -> Files -> Lab and Project - Materials and Submissions -> Lab 3 Submission (Late Submission)

Plagiarism is penalised with a 100% penalty for all SOURCES and RECIPIENTS

All past and future submissions, and marks, will be reviewed in greater detail, for any person found to have plagiarised

ALL THE SUBMISSION INSTRUCTIONS LISTED ABOVE WILL AFFECT YOUR GRADES!

GRADING PROCESS

- During subsequent lab sessions, our graders will be providing you updates on the grading of your submission
- Submissions not following all the **LUMINUS SUBMISSION INSTRUCTIONS** (listed above) will not be graded immediately, and will instead be reviewed towards the end of the semester. **You will not be able to see your results during the labs in such situations**

APPENDIX (Renaming submissions just before LumiNUS upload):

It is **compulsory to rename your project archive and report**, just before LumiNUS upload, as indicated in the table below. Copy your respective “Archive Naming” for the archive, and then replace the “xxxxxxxxxx” with your student ID number. Do not change any other part of the naming, except the “xxxxxxxxxx”.

Submission example for project archive: **L3_Fri_AM_Alan Turing_Archive_A0131086Z**

Name	Archive Naming
A AKIL AHAMED	L3 Fri AM A AKIL AHAMED Archive XXXXXXXXX
Abdul Hadi Bin Abdul Samad	L3 Fri AM Abdul Hadi Bin Abdul Archive XXXXXXXXX
Adabelle Lim Ru Leng	L3 Fri AM Adabelle Lim Ru Leng Archive XXXXXXXXX
Alfred Wrong Jia Qing	L3 Fri AM Alfred Wrong Jia Qin Archive XXXXXXXXX
Alvin Goh Jia Hao	L3 Fri AM Alvin Goh Jia Hao Archive XXXXXXXXX
Alvinci Merquita	L3 Wed AM Alvinci Merquita Archive XXXXXXXXX
ANG KENG SIANG	L3 Wed AM ANG KENG SIANG Archive XXXXXXXXX
Aryl Ng Shen Le	L3 Wed AM Aryl Ng Shen Le Archive XXXXXXXXX
Au Yuan Xian	L3 Fri AM Au Yuan Xian Archive XXXXXXXXX
Bai Xiaoru	L3 Fri AM Bai Xiaoru Archive XXXXXXXXX
Bryan Yu Cheng You	L3 Fri AM Bryan Yu Cheng You Archive XXXXXXXXX
Chai Wei Lynthia	L3 Fri AM Chai Wei Lynthia Archive XXXXXXXXX
Cheang Zhi Yi Jordan	L3 Fri AM Cheang Zhi Yi Jordan Archive XXXXXXXXX
Chee Poh Hock	L3 Wed AM Chee Poh Hock Archive XXXXXXXXX
Cheng Wei Qiao	L3 Fri AM Cheng Wei Qiao Archive XXXXXXXXX
Cheung Po Rui Bryan	L3 Fri AM Cheung Po Rui Bryan Archive XXXXXXXXX
CHONG LEE TENG VALENCIA	L3 Wed AM CHONG LEE TENG VALEN Archive XXXXXXXXX
Davian Chan Sze Peng	L3 Fri AM Davian Chan Sze Peng Archive XXXXXXXXX
David Michael Woodside	L3 Fri AM David Michael Woodsi Archive XXXXXXXXX
ELJER CHUA	L3 Fri AM ELJER CHUA Archive XXXXXXXXX
FANG XINJIA	L3 Fri AM FANG XINJIA Archive XXXXXXXXX
Fidel Tan Yan Sheng	L3 Fri AM Fidel Tan Yan Sheng Archive XXXXXXXXX
Foo Fang Kiang	L3 Fri AM Foo Fang Kiang Archive XXXXXXXXX
Gao Zhixuan	L3 Fri AM Gao Zhixuan Archive XXXXXXXXX
Giam Xiong Yao	L3 Fri AM Giam Xiong Yao Archive XXXXXXXXX
Gillian Ho Xin Ying	L3 Fri AM Gillian Ho Xin Ying Archive XXXXXXXXX
Goh Jia Hong Edwin	L3 Wed AM Goh Jia Hong Edwin Archive XXXXXXXXX
Guinne Teresa Sng Yu Lin	L3 Fri AM Guinne Teresa Sng Yu Archive XXXXXXXXX
Hariharan Hadrian S/O Subramaniam	L3 Fri AM Hariharan Hadrian S Archive XXXXXXXXX
HO MING JUN	L3 Wed AM HO MING JUN Archive XXXXXXXXX
Ho Yi Shu Keon	L3 Wed AM Ho Yi Shu Keon Archive XXXXXXXXX
Hou Yinjiayi	L3 Fri AM Hou Yinjiayi Archive XXXXXXXXX
Ian Isaiah Tan Jun Wei	L3 Fri AM Ian Isaiah Tan Jun W Archive XXXXXXXXX
Jacob Zhang Zhiqiang	L3 Wed AM Jacob Zhang Zhiqiang Archive XXXXXXXXX
JEROME TEO SZE YONG	L3 Wed AM JEROME TEO SZE YONG Archive XXXXXXXXX
Jonathan Ang Xu Wen	L3 Wed AM Jonathan Ang Xu Wen Archive XXXXXXXXX
JONATHAN KHOO TENG YANG	L3 Fri AM JONATHAN KHOO TENG Y Archive XXXXXXXXX
Kabeta Takuma	L3 Wed AM Kabeta Takuma Archive XXXXXXXXX
Khoo Wu Jian Samuel	L3 Wed AM Khoo Wu Jian Samuel Archive XXXXXXXXX
KIM JOOHWAN	L3 Fri AM KIM JOOHWAN Archive XXXXXXXXX
Lau Wai Kit	L3 Wed AM Lau Wai Kit Archive XXXXXXXXX
LEE KE HUI	L3 Wed AM LEE KE HUI Archive XXXXXXXXX
Lee Shao Yu	L3 Wed AM Lee Shao Yu Archive XXXXXXXXX
Lek Ju Ying	L3 Wed AM Lek Ju Ying Archive XXXXXXXXX
Leong Ka Weng, Rachelle	L3 Fri AM Leong Ka Weng Rache Archive XXXXXXXXX
LEW POH CHEN, DOUGLAS	L3 Fri AM LEW POH CHEN DOUGLA Archive XXXXXXXXX
Long Deng Jie	L3 Wed AM Long Deng Jie Archive XXXXXXXXX
Markus Lim Yi Qin	L3 Wed AM Markus Lim Yi Qin Archive XXXXXXXXX
Mohamad Adam Bin Mohamad Yazid	L3 Wed AM Mohamad Adam Bin Moh Archive XXXXXXXXX
Muhammad Irfan Bin Zakaria	L3 Wed AM Muhammad Irfan Bin Z Archive XXXXXXXXX
Myat Thwe Naing	L3 Wed AM Myat Thwe Naing Archive XXXXXXXXX
Ng Etek	L3 Wed AM Ng Etek Archive XXXXXXXXX
Noorhakim Bin Jasman	L3 Wed AM Noorhakim Bin Jasman Archive XXXXXXXXX
NUR SYADIAH BTE LUTFI	L3 Fri AM NUR SYADIAH BTE LUT Archive XXXXXXXXX
ONG WEI SHENG	L3 Fri AM ONG WEI SHENG Archive XXXXXXXXX
PANG JUN WEN, ADRIC	L3 Fri AM PANG JUN WEN ADRIC Archive XXXXXXXXX
PUN ZE YONG	L3 Wed AM PUN ZE YONG Archive XXXXXXXXX
Qiang Zhuang	L3 Wed AM Qiang Zhuang Archive XXXXXXXXX
QIU YI WEN	L3 Fri AM QIU YI WEN Archive XXXXXXXXX
R M RAAJAMANI	L3 Fri AM R M RAAJAMANI Archive XXXXXXXXX
RIZAVUR RAHMAN FASLUR RAHMAN	L3 Fri AM RIZAVUR RAHMAN FASLU Archive XXXXXXXXX
Ryan Tan Jun Hao	L3 Wed AM Ryan Tan Jun Hao Archive XXXXXXXXX
Saw Wee Kiat	L3 Wed AM Saw Wee Kiat Archive XXXXXXXXX
SIM BOWEN	L3 Fri AM SIM BOWEN Archive XXXXXXXXX
TAM LI NA	L3 Fri AM TAM LI NA Archive XXXXXXXXX
Tan Javen	L3 Wed AM Tan Javen Archive XXXXXXXXX
Tan Kai Hao Andrew	L3 Wed AM Tan Kai Hao Andrew Archive XXXXXXXXX
Tan Suet Ying	L3 Fri AM Tan Suet Ying Archive XXXXXXXXX
Tan Yeung Ming Sean Eugene	L3 Wed AM Tan Yeung Ming Sean Archive XXXXXXXXX
Teoh Yi Zheng	L3 Fri AM Teoh Yi Zheng Archive XXXXXXXXX
Tey Zi Le	L3 Wed AM Tey Zi Le Archive XXXXXXXXX
Thet Ke Min, Sonia	L3 Wed AM Thet Ke Min Sonia Archive XXXXXXXXX
Trina Wern Qin Rong	L3 Fri AM Trina Wern Qin Rong Archive XXXXXXXXX
Venessa Chee Li Lin	L3 Fri AM Venessa Chee Li Lin Archive XXXXXXXXX
WANG HUA CHEN	L3 Fri AM WANG HUA CHEN Archive XXXXXXXXX
Wee Cheng Yuan Andrew	L3 Wed AM Wee Cheng Yuan Andre Archive XXXXXXXXX
Wee Xin Ze	L3 Wed AM Wee Xin Ze Archive XXXXXXXXX
Yeo Zhong Kang Dennis	L3 Wed AM Yeo Zhong Kang Denni Archive XXXXXXXXX
ZHONG SHUHAO	L3 Fri AM ZHONG SHUHAO Archive XXXXXXXXX